


We only care for the ② flag!

Code	Suffix	Flags	Meaning
0000	EQ	Z set	equal
0001	NE	Z clear	not equal
0010	CS	C set	unsigned higher or same
0011	CC	C clear	unsigned lower
0100	MI	N set	negative
0101	PL	N clear	positive or zero
0110	VS	V set	overflow
0111	VC	V clear	no overflow
1000	HI	C set and Z clear	unsigned higher
1001	LS	C clear or Z set	unsigned lower or same
1010	GE	N equals V	greater or equal
1011	LT	N not equal to V	less than
1100	GT	Z clear AND (N equals V)	greater than
1101	LE	Z set OR (N not equal to V)	less than or equal
1110	AL	(ignored)	always


ISA to be implemented ...

Mnemonic	Name		Operation
ADD	Addition	add Rd,Rn,Rm	$Rd \leftarrow Rn + (Rm \text{ sh } \text{shamt}5)$
SUB	Subtraction	sub Rd,Rn,Rm	$Rd \leftarrow Rn - (Rm \text{ sh } \text{shamt}5)$
AND	Bitwise And	and Rd,Rn,Rm	$Rd \leftarrow Rn \& (Rm \text{ sh } \text{shamt}5)$
ORR	Bitwise Or	orr Rd,Rn,Rm	$Rd \leftarrow Rn (Rm \text{ sh } \text{shamt}5)$
MOV	Move to Register	mov Rd,Rm	$Rd \leftarrow (Rm \text{ sh } \text{shamt}5)$
STR	Store	str Rd,[Rn,imm12]	$\text{Mem}[Rn + \text{imm}12] \leftarrow Rd$
LDR	Load	ldr Rd,[Rn,imm12]	$Rd \leftarrow \text{Mem}[Rn + \text{imm}12]$
CMP	Compare	cmp Rd,Rn,Rm	set the flag if $(Rn - Rm = 0)$
B	Branch	b imm24	$PC \leftarrow \text{imm}24$
BEQ	Branch if Equal	beq imm24	$PC \leftarrow \text{imm}24$ if flag = 1
BL	Branch with Link	bl imm24	$PC \leftarrow \text{imm}24, R14 \leftarrow PC$
BX	Branch and Exchange	bx Rm	$PC \leftarrow Rm$

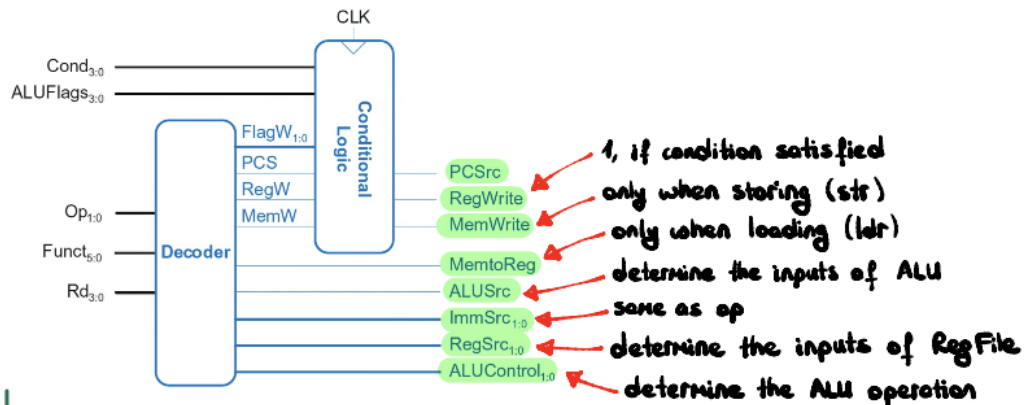We have to determine the control signals for each instruction.



ISA	PCSrc	RegWrite	MemWrite	MemtoReg	ALUSrc	ImmSrc	RegSrc	ALUctrl
ADD	0	1 if cond	0	0	0	00	00	0100
SUB	0	1 if cond	0	0	0	00	00	0010
AND	0	1 if cond	0	0	0	00	00	0000
ORR	0	1 if cond	0	0	0	00	00	1100
MOV	0	1 if cond	0	0	0	00	0X	1101
STR	0	0	1 if cond	0	1	01	10	0100
LDR	0	1 if cond	0	1	1	01	X0	0100
CMP	0	0	0	0	0	XX	00	0010
B	1	0	0	0	1	10	XX	1101
BEQ	1	0	0	0	1	10	XX	1101
BL	1	0	0	0	1	10	X1	1101
BX	1	0	0	0	0	10	0X	1101

 

Datapath is tested with following instructions...

LDR R5, R2; $R2=0, R5 \leftarrow \text{Mem}[0]=4$

after this instruction, $R5 = 4$

LDR R6, R2, #4; $R6 \leftarrow \text{Mem}[0+4]=7$

after this instruction, $R6 = 7$

ADD R7, R6, R5; $R7 \leftarrow R5 + R6$

after this instruction, $R7 = 11$

SUB R8, R6, R5; $R8 \leftarrow R6 - R5$

after this instruction, $R8 = 3$

STR R8, R2, #12; $R8 \rightarrow \text{Mem}[0+12]$

at memory loc. 12, 3 is written

LDR R0, R2, #12; $R0 \leftarrow \text{Mem}[0+12]=3$

after this instruction, $R0 = 3$

ORR R3, R0, R5; $R3 \leftarrow (0011) | (0100)$

after this instruction, $R3 = 0111$

AND R4, R3, R0, #2; $R4 \leftarrow (0111) \& (1100)$

after this instruction, $R4 = 0100$

MOV R1, R4, #2; $R1 \leftarrow (4 \times 2^2) \leftarrow \text{shift}$

after this instruction, $R1 = 10000$

B #64; $PC \leftarrow 64$

after this instruction, $PC = 64$

Following pages have cocotb terminal results of these instructions for the datapath.



```

### TESTING THE DATAPATH ###
### READING THE INSTRUCTIONS FROM inst_mem.txt ###
PC: 00000000000000000000000000000000
~~~~~

```

Testing LDR Operation...

LDR R5, R2;

```

R2 = 0, mem[0] = 4, Write 4 to R5
PC: 00000000000000000000000000000000
Instr: 11100100000000100101000000000000
PCSrc: 0
Reg_Write: 1
Mem_Write: 0
MementoReg: 1
ALUSrc: 1
ImmSrc: 01
RegSrc: 00
ALUControl: 0100
RA1: 0010
RA2: 0000
ALUResult: 00000000000000000000000000000000
ReadData: 00000000000000000000000000000100
MementoRegResult: 00000000000000000000000000000100
### End of Instruction ###
~~~~~

```

Testing LDR Operation...

LDR R6, R2, #4;

```

R2 = 0, mem[4] = 7, Write 7 to R6
PC: 00000000000000000000000000000100
Instr: 11100100000000100110000000000100
PCSrc: 0
Reg_Write: 1
Mem_Write: 0
MementoReg: 1
ALUSrc: 1
ImmSrc: 01
RegSrc: 00
ALUControl: 0100
RA1: 0010
RA2: 0100
ALUResult: 00000000000000000000000000000100
ReadData: 00000000000000000000000000000111
MementoRegResult: 00000000000000000000000000000111
### End of Instruction ###
~~~~~

```

Testing ADD Operation...

ADD R7, R6, R5;

```

Write R5 + R6 (4+7) to R7 (11).
PC: 00000000000000000000000000000100
Instr: 11100000100001100111000000000101
PCSrc: 0
Reg_Write: 1
Mem_Write: 0
MementoReg: 0
ALUSrc: 0
ImmSrc: 00
RegSrc: 00
ALUControl: 0100
RA1: 0110
RA2: 0101
ALUResult: 00000000000000000000000000000111
ReadData: 00000000000000000000000000000000
MementoRegResult: 00000000000000000000000000000111
2 LDR and 1 ADD operations done successfully.
### End of Instruction ###
~~~~~

```

Testing SUB Operation...

SUB R8, R6, R5;

```

Write R6 - R5 (7-4) to R8 (3).
PC: 00000000000000000000000000000100
Instr: 11100000100001101000000000000101
PCSrc: 0
Reg_Write: 1
Mem_Write: 0
MementoReg: 0
ALUSrc: 0
ImmSrc: 00
RegSrc: 00
ALUControl: 0010
RA1: 0110
RA2: 0101
ALUResult: 00000000000000000000000000000011
ReadData: 00000000000000000000000000000000
MementoRegResult: 00000000000000000000000000000011
SUB operation done successfully.
### End of Instruction ###
~~~~~

```

Testing STR Operation...

STR R8 (3), R2, #12;

3 is written in R8

```

Store value of R8 in the memory address [R2] (which is zero) added 12 (mem[12]).
PC: 00000000000000000000000000000000
PCSrc: 0
Reg_Write: 0
Mem_Write: 1
MementoReg: 0
ALUSrc: 1
ImmSrc: 01
RegSrc: 10
ALUControl: 0100
RA1: 0000
RA2: 1000
ALUResult: 00000000000000000000000000000100
ReadData: 00000000000000000000000000000000
MementoRegResult: 00000000000000000000000000000100
### End of Instruction ###
~~~~~

```

Testing LDR Operation...

LDR R0, R2, #12;

```

R2 = 0, mem[0+12] = 3, Write 3 to R0
PC: 00000000000000000000000000000100
PCSrc: 0
Reg_Write: 1
Mem_Write: 0
MementoReg: 1
ALUSrc: 1
ImmSrc: 01
RegSrc: 00
ALUControl: 0100
RA1: 0010
RA2: 1100
ALUResult: 00000000000000000000000000000011
ReadData: 00000000000000000000000000000011
MementoRegResult: 00000000000000000000000000000011
1 STR and 1 LDR operations done successfully
### End of Instruction ###
~~~~~

```

PC must be 20 after 5 instructions

Testing ORR Operation...

ORR R3, R0, R5;

PC must be 20 after 5 instructions

Testing ORR Operation...

ORR R3, R0, R5;

```

Write (0011) or (0100) = (0111) to R3.
PC: 00000000000000000000000000000100
PCSrc: 0
Reg_Write: 1
Mem_Write: 0
MementoReg: 0
ALUSrc: 0
ImmSrc: 00
RegSrc: 00
ALUControl: 1100
RA1: 0000
RA2: 0101
ALUResult: 00000000000000000000000000000111
ReadData: 00000000000000000000000000000000
MementoRegResult: 00000000000000000000000000000111
7 is written to R3.
### End of Instruction ###
~~~~~

```

Testing AND Operation...

AND R4, R3, R0, #3;

```

Write (0111) and (1100) = (0100) to R4.
PC: 000000000000000000000000000001100
PCSrc: 0
Reg_Write: 1
Mem_Write: 0
MementoReg: 0
ALUSrc: 0
ImmSrc: 00
RegSrc: 00
ALUControl: 0000
RA1: 0011
RA2: 0000
ALUResult: 00000000000000000000000000000100
ReadData: 00000000000000000000000000000111
MementoRegResult: 00000000000000000000000000000100
4 is written to R4.
### End of Instruction ###
~~~~~

```

PC: 40 -> 64

Result is not written in R2 since condition is not satisfied.

[illegible]

```
PCSrc: 0
RegWrite: 0
MemWrite: 0
MemtoReg: 0
ALUSrc: 0
ImmSrc: 00
RegSrc: 00
ALUControl: 0100
```

Flag Z: 0

```
### End of Instruction ###
```

Testing ADD Operation...

```
ADD R6, R2, R1;
```

[illegible]

```
PCSrc: 0
RegWrite: 1
MemWrite: 0
MemtoReg: 0
ALUSrc: 0
ImmSrc: 00
RegSrc: 00
ALUControl: 0100
```

Flag Z: 0

```
### End of Instruction ###
```

2's Complement Subroutine is at memory location 40.

```
Testing SUB Operation...

SUB R0, R1, R0;

NOT R0

PC: 0000000000000000000000000101000
Instr: 1110000010000010000000000000000
RA1: 0001
RA2: 0000
RD1: 0000000000000000000000000000000
RD2: 11111111111111111111111111111100
ALUResult: 0000000000000000000000000000100
result: 0000000000000000000000000000100

PCSrc: 0
RegWrite: 1
MemWrite: 0
MemtoReg: 0
ALUSrc: 0
ImmSrc: 00
RegSrc: 00
ALUControl: 0010

2's Complement Operation is successful. !!!
### End of Instruction ###

~~~~~

Testing STR Operation...

STR R0 , R1, #8;

PC: 0000000000000000000000000101100
Instr: 1110010000000001000000000001000
RA1: 0001
RA2: 0000
RD1: 0000000000000000000000000000000
RD2: 00000000000000000000000000000100
ALUResult: 00000000000000000000000000001000
result: 00000000000000000000000000001000

PCSrc: 0
RegWrite: 0
MemWrite: 1
MemtoReg: 0
ALUSrc: 1
ImmSrc: 01
RegSrc: 10
ALUControl: 0100

2's Complement is stored at memory location 4. !!!
2's Complement subroutine is at memory location 40

### End of Instruction ###

~~~~~
```

You can see main_COCO file for more examples.

Adding the numbers, 17,25,4...
And, obtained 46 as result after 3 loops.

[illegible]

```
PCSrc: 1
RegWrite: 0
MemWrite: 0
MemtoReg: 0
ALUSrc: 1
ImmSrc: 10
RegSrc: 00
ALUControl: 1101
```

Flag Z: 0

=====

```
LDR R5, R4 #4;
```

R0 = 0, mem[8] = 4, Write 4 to R2

```
PC: 0000000000000000000000000000000010000
Instr: 111001000000101000101000000000100
RA1: 0100
RA2: 0100
RD1: 0000000000000000000000000000010100
RD2: 0000000000000000000000000000010100
ALUResult: 00000000000000000000000000001100
result: 00000000000000000000000000000100
```

```
PCSrc: 0
RegWrite: 1
MemWrite: 0
MemtoReg: 1
ALUSrc: 1
ImmSrc: 01
RegSrc: 00
ALUControl: 0100
```

Flag Z: 0

```
ADD R10, R5 R10;
```

R0 = 0, mem[8] = 4, Write 4 to R2

[illegible]

Starting the sum from the address 16.

```
C: > Users > ardaunver > Desktop > EE446PRE2 > MainCoco2  
1 01  
2 00  
3 00  
4 00  
5 03  
6 00  
7 00  
8 00  
9 04  
10 00  
11 00  
12 00  
13 0C  
14 00  
15 00  
16 00  
17 11  
18 00  
19 00  
20 00  
21 19  
22 00  
23 00  
24 00  
25 04  
26 00  
27 00  
28 00
```